

3E1642

Roll No. _____

[Total No. of Pages : 3]

3E1642

B.Tech. III Sem.(Main/Back) Examination, Dec. - 2016

Electrical Engineering
3EE2A Circuit Analysis - I

Time : 3 Hours


Maximum Marks : 80
Min. Passing Marks : 26

Instructions to Candidates:

Attempt any **five** questions, selecting one question from **each** unit. All questions carry equal marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.


Unit - I

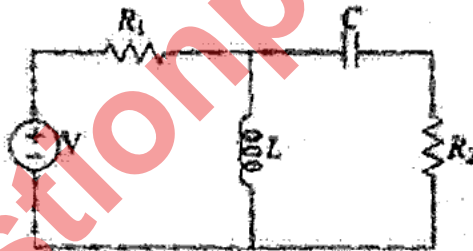1. a) Define Q factor in an AC circuit. Deduce the relation between band width, resonant frequency and Q factor. (8)
- b) Draw the dual of the network shown in figure. (8)



OR

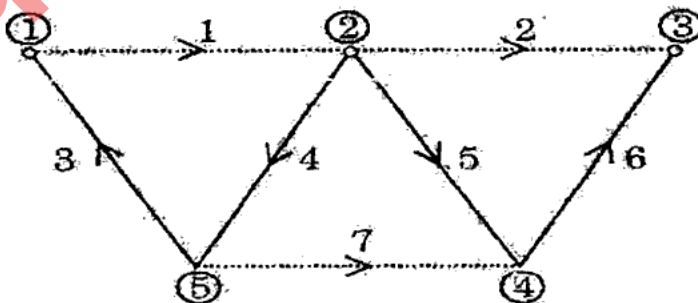
1. a) A graph is shown in figure below. Find the tie - set and cut set matrices and obtain the KCL and KVL equations. (8)



- b) A 240-V, 100-Hz ac source is connected to a series RLC circuit consisting of a coil and variable capacitor. The coil has a resistance of $55\text{ m}\Omega$ and an inductance of 7 mH . The capacitor is varied so as to achieve resonance. Determine (i) the value of the capacitance, (ii) the circuit quality factor, and (iii) the half - power frequencies. (8)

Unit - II

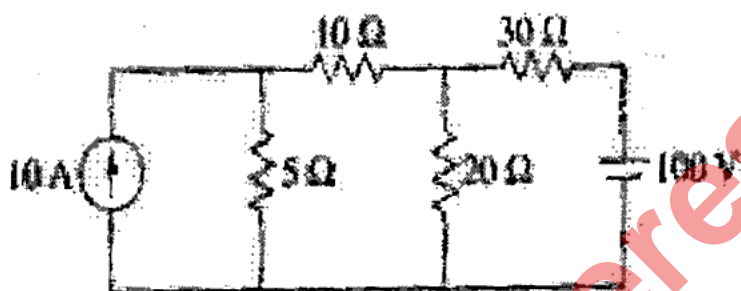2. a) Using Thevenin Theorem, find the current through the $10\text{-}\Omega$ resistor. (8)



- b) State and explain for Tellegen's theorem that the sum of power delivered to a closed network is zero. (8)

OR

2. a) State and explain for maximum power transfer theorem that power transfer from a d.c. source network to a resistive network is maximum when the internal resistance of the d.c. source network is equal to the load resistance. (8)
- b) Explain the compensation theorem with its limitations. (8)

Unit - III


3. a) A balanced, three - phase load connected in delta draws a power of 10.4 kW at 200 V at a power factor of 0.5 lead. Find the values of the circuit elements and the reactive voltamperes drawn. (8)
- b) What do you mean by power triangle? Explain active, reactive and apparent power with example. (8)

OR

3. a) Explain the neat circuit and phasor diagram, how the power and power factor of $3\text{-}\phi$ system can be measured by means of two wattmeter method. (8)
- b) Write down the relationship between line voltage and line current with phase voltage and phase current in star connected and delta connected circuits. (8)

Unit - IV

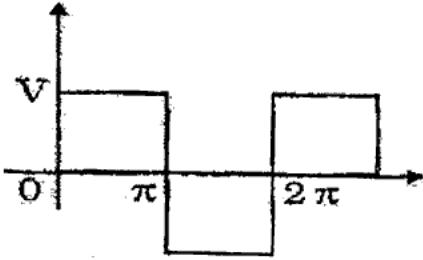4. a) A square waveform is shown below. Obtain the Fourier series. (8)



- b) Derive the expression of power with Non - sinusoidal voltage and current. (8)

OR

4. a) Find the first few terms of Fourier series of the function given by

$$f(a) = 1 \text{ for } 0 < a < \pi$$

$$f(a) = -1 \text{ for } \pi < a < 2\pi$$

(8)

- b) Explain the different kinds of symmetry in non - sinusoidal waves. (8)

Unit - V

5. a) A 50 Hz, 400 V (peak value) sinusoidal voltage is applied at $t = 0$ to a series R-L circuit having resistance 5Ω and inductance 0.2 H. Obtain an expression of current at any instant t . Calculate the value of the transient current 0.1 sec. after switching on. rtuonline.com (8)
- b) State and deduce initial - value and final value theorems. (8)

OR

5. a) Explain the impulse response of series RC network. (8)
- b) An impulse function is given by $s(t-t_1)$. Obtain its Laplace transform. (8)

