

4E 4172


B.Tech. IV Semester (Main) Examination, June/July - 2015
Electrical Engineering
4EE2A Circuit Analysis-II

Time : 3 Hours**Maximum Marks : 80**
Min. Passing Marks : 26**Instructions to Candidates:**


Attempt any **five** questions, selecting **one** question from **each unit**. All questions carry **equal** marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Unit - I

1. Explain the physical interpretation of complex frequency (6)
2. Analysis the circuit on loop current basis & hence find I_1, I_2 & I_3 (10)

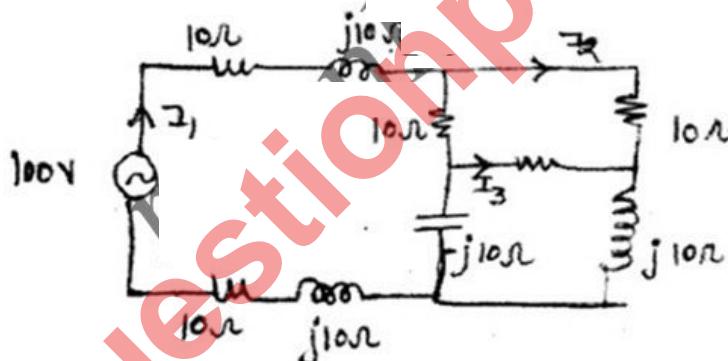**OR**

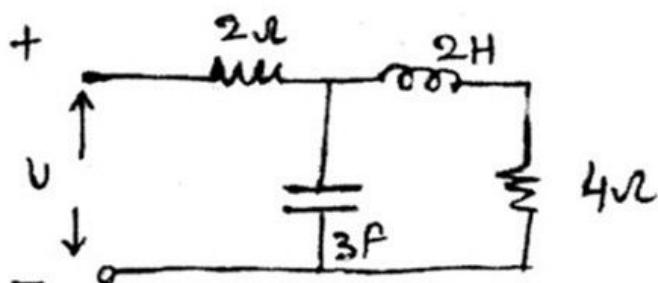
1. For the given network determine the transform impedance (8)



2. Obtain the transform admittance of the inductor by using time domain relationship of voltage & current (8)

Unit - II

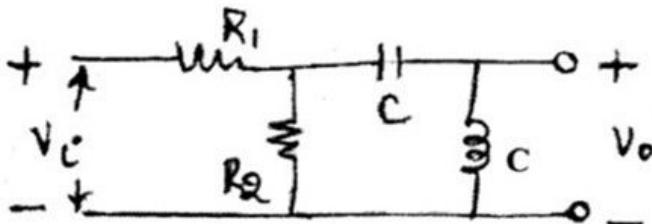1. Determine the $\frac{V_c(s)}{V_i(s)}$ of network shown below (8)



2. Find the time domain response for the network function $I(s) = \frac{3s(s+2)}{(s+1)(s+4)}$ (8)

OR

1. Show the effects of pole position on stability (8)
2. Check the stability of $p(s) = s^4 + 2s^3 + 4s^2 + 12s + 10$ (8)

Unit - III

1. Obtain foster I & foster II form for $Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$ (16)


OR

1. Write down the properties of RC impedance function (8)
2. Check whether the given function is positive real function or not (8)

$$Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

Unit - IV

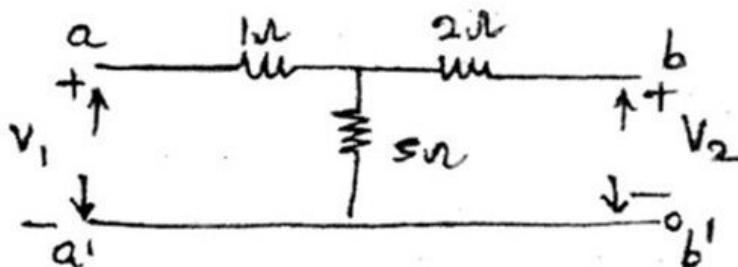1. Find the transmission parameters for the given circuit (8)




2. Derive the condition of reciprocity and symmetry in Z parameters

(8)

OR


1. Explain image impedance calculate the value of image impedance of the following network

(8)

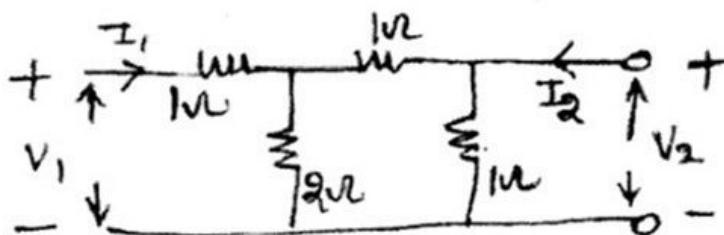

2. Find h - parameters of the network shown in figure

(8)

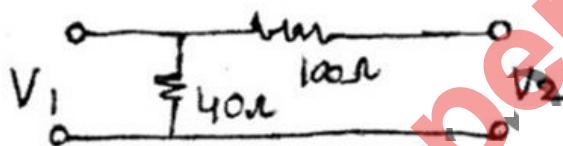

Unit - V

1. Derive the value of characteristic impedance for a T type constant k low pass filter

(8)

2. Write a short note on active filters

(8)

OR

1. Design a π section of m-derived Hpf having design impedance of 600Ω cut off frequency 4kHz and infinite attenuation at 3.6KHz

(8)

2. What do you understand by lattice filter. How a ladder filter network can be converted into lattice filter. find the cut off frequency for same

(8)