

4E2109

Roll No. _____

Total No of Pages: 7

4E2109

B. Tech. IV Sem. (Back) Exam., June/July-2014

Electrical Engineering
4EE1 Power Electronics II

Time: 3 Hours

Maximum Marks: 80

Min. Passing Marks: 24

Instructions to Candidates:-

Attempt any **five** questions, selecting **one** question from each unit. All Questions carry **equal** marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.

Units of quantities used/ calculated must be stated clearly.


Use of following supporting material is permitted during examination.

1. _____

2. _____

UNIT-I

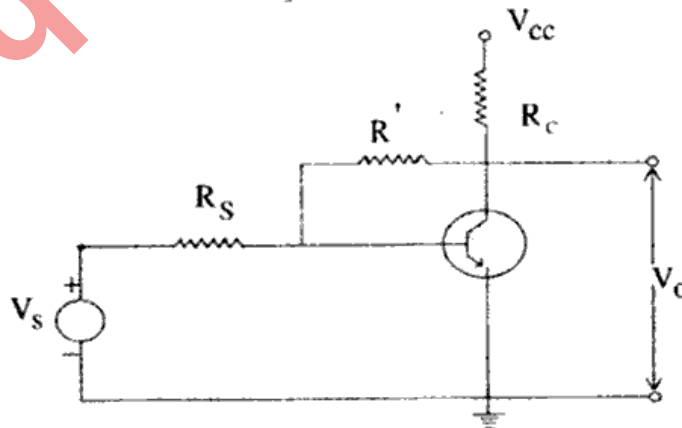- Q.1. (a) Identify the topology in the circuit. Prove that the voltage of the amplifier with feedback is given by $-\frac{R'}{R_s}$ [8]



[4E2109]

Page 1 of 7

[3560]

- (b) List five characteristics of an amplifier which are modified by negative feedback.


Explain them in brief.

[8]

OR

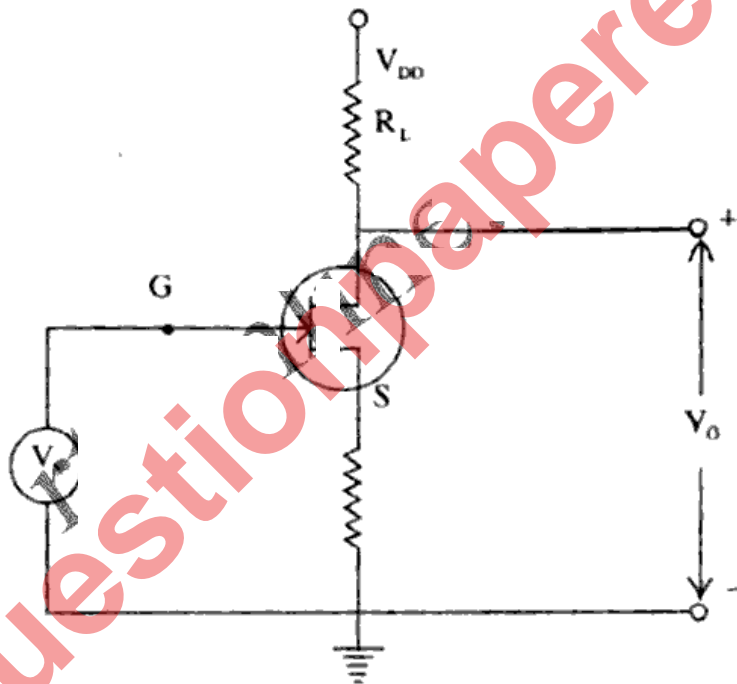- Q.1. (a) Draw the equivalent circuit of the following amplifier and show that the output resistance with load resistance R_L with feedback is - [10]

$$R'_{of} = \frac{R_L [r_d + (\mu + 1)R]}{r_d + R_L + (\mu + 1)R}$$



- (b) Distinguish between voltage series and current series. Explain briefly with suitable circuit diagram. [6]

- (b) List five characteristics of an amplifier which are modified by negative feedback.


Explain them in brief.

[8]

OR

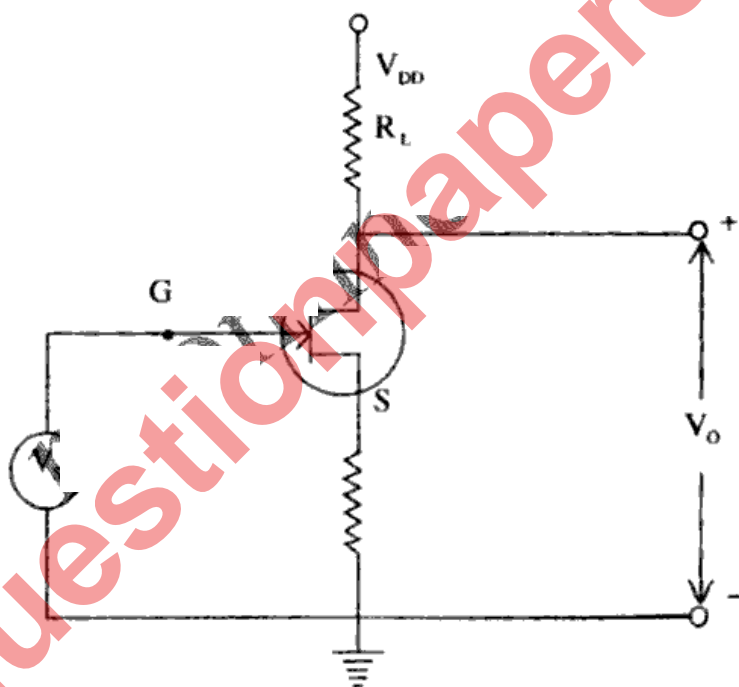- Q.1. (a) Draw the equivalent circuit of the following amplifier and show that the output resistance with load resistance R_L with feedback is - [10]

$$R'_{of} = \frac{R_L [r_d + (\mu + 1)R]}{r_d + R_L + (\mu + 1)R}$$



- (b) Distinguish between voltage series and current series. Explain briefly with suitable circuit diagram. [6]

UNIT-II


- Q.2. (a) Sketch the topology for a generalised resonant circuit oscillator, using impedance $Z_1 Z_2 Z_3$. At what frequency will the circuit oscillate? Under what conditions does the configuration reduces to Hartley Oscillator? [8]
- (b) What is Schmitt triggering? Explain the working of a Schmitt trigger with the help of a neat circuit diagram and waveform. [8]

OR

- Q.2. (a) Explain the Barkhausen criterion for sustained oscillation. An FET RC phase shift oscillator is required to oscillate at 1 KHz. JFET used has $g_m = 5 \text{ mA/V}$ and $r_d = 20 \text{ k}\Omega$. If $R = 10 \text{ k}\Omega$ find the value of
- (i) Capacitance in RC network.
- (ii) External load resistance R_D . [8]
- (b) Normally, crystal controlled oscillator are not available beyond 10 MHz. Why? [4]
- (c) Explain the working of BJT bistable multi vibrator. [4]

UNIT-III

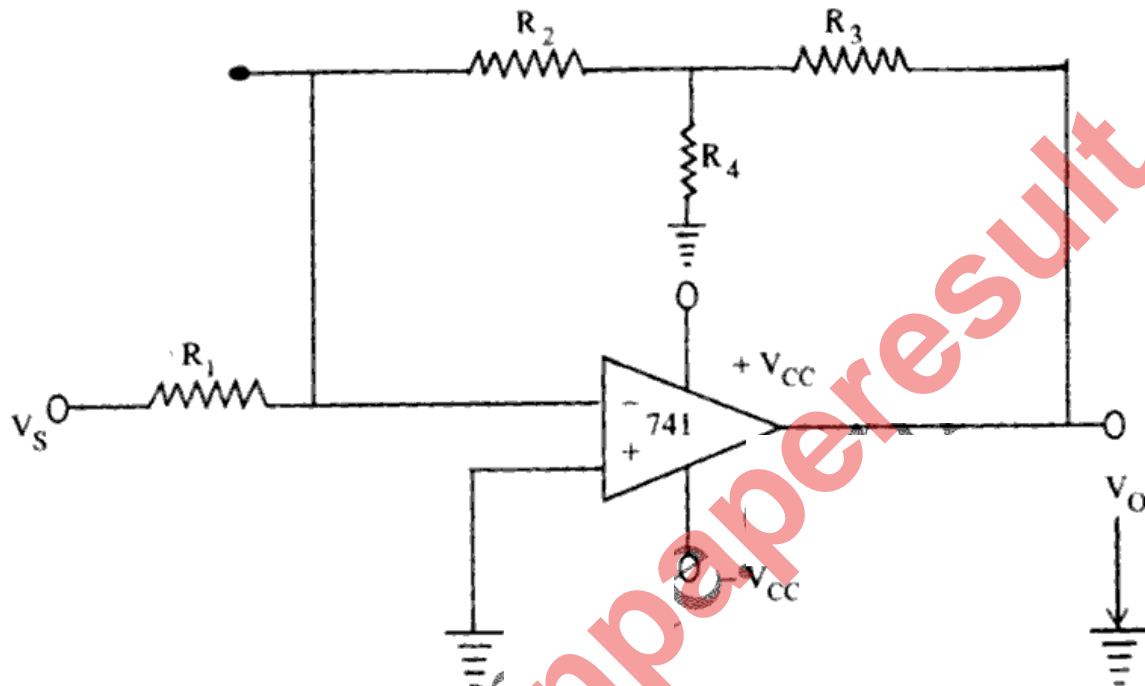- Q.3. (a) Find V_o/V_s for the circuit in figure. Use $R_1 = 5 \text{ K}\Omega$, $R_2 = R_3 = 20 \text{ K}\Omega$ and $R_4 = 1 \text{ K}\Omega$ [8]



- (b) Write short note on -

- (i) Logarithmic amplifier using op-amp
- (ii) Differentiator

OR

Q.3. (a) Define following parameters in brief -

[8]

- (i) Slew Rate
 - (ii) CMRR
 - (iii) Input Offset Voltage
 - (iv) PSRR
 - (v) Input Offset current drift.
- (b) Explain the operation of Integrator using op - amp and also draw input and output wave from.

[8]

UNIT-IV

Q.4. (a) Explain a monostable multivibrator using Ic - 555 with functional block diagram of Ic.

[8]

(b) Connect Ic-555 as astable multivibrator with following particulars-


$R_A = R_B = 7.5 \text{ K}\Omega$, $C = 0.1 \mu\text{F}$, $V_{cc} = 5\text{V}$. Find output frequency.

[8]

OR

Q.4. (a) Explain working of precision half wave and full wave rectifier using op-amp- 741. [8]

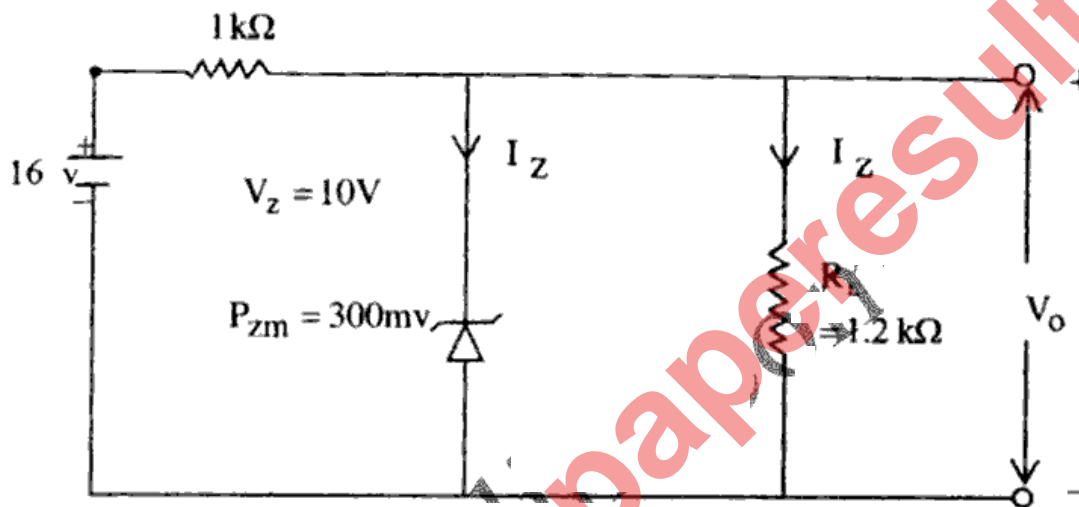(b) For Zener circuit calculate V_L , V_R , I_Z , P_Z [8]



UNIT-V

Q.5. (a) In a class – B push pull amplifier, prove that

$$P_{cmax} = \frac{4}{\pi^2} P_{max} \quad [8]$$

(b) What is meant by cross over distortion in class – B amplifier. Explain how it is overcome in class – AB operation? [4]

- (c) Discuss the classification of amplifiers based on Function, Frequency, Conduction angle, Type of coupling and Load. [4]

OR

- Q.5 (a) Draw the schematic circuit diagram of series fed class – A amplifier and explain its working. [8]

- (b) A sinusoidal signal $V_s = 1.95 \sin 400t$ is applied to a power amplifier, the resultant current is

$$i_o = 12 \sin 400t + 1.2 \sin 800t + 0.9 \sin 1200t + 0.4 \sin 1600t$$

Calculate

- (i) Total harmonic distortion
- (ii) The percentage increase in power because of distortion. [4]
- (c) Show the classification of power amplifier using output characteristics load line and operating point. [4]
