

B.Tech. VI Semester (Main/Back) Examination, May-June 2015

Electrical & Electronics Engineering

6EE4A Advanced power Electronics

Common for EE,EX

Time : 3 Hours

Maximum Marks : 80

Min. Passing Marks : 24

Instructions to Candidates:

Attempt any **five** questions, selecting **one** question from **each** unit. All questions carry **equal** marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Unit - I

1. a) Explain on - off control and phase angle control of 1- ϕ Ac voltage controller with R-Load. (8)
- b) A single phase Ac voltage controller has resistive load of 10Ω input voltage $V_s = 120\text{V}$, 60Hz the delay angle of thyristor T_1 is $\alpha = \frac{\pi}{2}$ determine.
 - i) RMS value of output voltage.
 - ii) Input power factor. (4+4)

OR

1. Explain the three phase full wave controller with star connected resistive load also draw wave forms. (16)

Unit - II

2. a) Describe 3 - phase to three phase cycloconverter with relevant circuit using 18 SCRs and 36 SCRs. (10)

- b) What are the advantage of 3- ϕ bridge circuit cycloconverter over 18- thyristor device. (6)

OR

2. a) Describe the basic working principle of single phase to single phase step down cycloconverter continuous conduction for bridge type cycloconverter. (8)

- b) Show that the fundamental RMS value of per phase output voltage of low frequency for an M - pulse converter is given by $V_{or} = V_{pn} \left(\frac{M}{\pi} \right) \sin \left(\frac{\pi}{M} \right)$. (8)

Unit - III

3. a) A single phase full bridge inverter inconnected to a dc source of V_s , resolve the o/p voltage wave shape into fourier series. (8)
- b) Explain working principle of three phase bridge inverter with 180° degree of conduction. (8)

OR

3. a) What is pulse width modulation? List the various PWM techniques, How do these differ from each other. (8)
- b) For a single pulse modulation used in inverters show that output voltage can be expressed as $V_p = \sum_{n=1,3,5} \frac{4V_s}{n\pi} \sin \left(\frac{n\pi}{2} \right) \sin nd \sin(n\omega t)$, where 2d is pulse width. (8)

Unit - IV

4. a) Explain working of L - type ZCS resonant converter. (8)
- b) The 2cs resonant converter deliner maximum power of $w/P_L = 400mw$ at $V_0 = 4v$ the supply voltage $V_s = 12v$. The maximum operating frequency 50Hz. Determine the value of L and C assume t_1 and t_3 are very small and $x = 1.5$. (8)

OR

4. a) Write down short note on ZVS resonant converter. (10)
- b) Write down the advantages and Limitations of ZVS. (6)

Unit - V

5. a) Explain the control circuit of current mode control and voltage mode control. (8)
- b) write down short note on multistage conversion. (8)

OR

5. a) What is the switched mode Dc power supplies. Explain working principle of flyback converter. (8)
- b) Explain the operation of full bridge converter. (8)