

6E3111

Roll No. \_\_\_\_\_

Total No of Pages: **4**

**6E3111**

**B.Tech VI Sem. (Main & Back) Exam., May. 2013**

**Electrical Engg.**

**6EE 3 Protection of Power Systems**

**Time: 3 Hours**

**Maximum Marks: 80**

**Min. Passing Marks: 24**

*Instructions to Candidates:*

*Attempt any **five** questions, selecting **one** question from **each** unit. All questions carry **equal** marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.*

*Units of quantities used/calculated must be stated clearly.*

*Use of following supporting material is permitted during examination.*

*(Mentioned in form No. 205)*

1. \_\_\_\_\_

2. \_\_\_\_\_

### **UNIT – I**

- Q.1. (a) Explain what are primary protection and back-up protection? Discuss the remote back-up protection by Simple time graded relays. [8]
- (b) Explain the following Scheme's with basic requirement of protection system, used in Circuit Breakers.
- (i) Trip circuit with relay of make type contact.
- (ii) Trip circuit with relay of brake type contact. [8]

**OR**

[6E3111]

Page 1 of 4

[10020]

- Q.1. (a) Describe the transient errors in current Transformer. [8]
- (b) A particular bar type current transformer has 300 secondary turns. The secondary winding carries a burden of ammeter having resistance of  $1\Omega$  and inductive reactance of  $0.53\Omega$ , while secondary winding resistance is  $0.25\Omega$  and reactance  $0.35\Omega$ . The magnetising mmf. required is 85A; while current component for core losses is 50A. Find [8]
- The primary current when secondary carries 5A.
  - The ratio error.
  - The reduction in the number of turns of secondary to obtain zero ratio error.

## UNIT – II

- Q.2. (a) Explain with the help of neat sketch, the principle, construction and working of directional induction type overcurrent relay. [rtuonline.com](http://rtuonline.com) [8]
- (b) The current rating of an overcurrent relay is 5A. It has PMS=2; TSM=0.3, CT ratio is 400/5; fault current = 4000A. Determine the time of operation of the relay assuming normal IDMT characteristics. [8]

PSM	2	4	5	8	10	20
Operating Time (s)	10	5	4	3	2.8	2.4

## OR

- Q.2. (a) To use the directional relay what are the conditions to be satisfied? Explain briefly. [7]
- (b) Describe the combined "Current and time" grading protective scheme of overcurrent relays. How the protection of ring-main feeder is provided by directional and non-directional over current relay. [9]

### UNIT – III

- Q.3. (a) Draw and Explain the Merz-Price protection of Alternator Stator Winding - State its advantages. [7]
- (b) Explain, with the aid of neat diagram of connections, the principle of operations of current balance type differential protection of generator against earth and inter phase fault. [9]

#### OR

- Q.3. (a) Which are the various abnormal running conditions which may exist in generator? What are their effects and how these effects can be minimized? [9]
- (b) Why restricted earth fault protection is provided to alternators through it leaves a portion of winding unprotected against earth fault. Justified? [7]

### UNIT – IV

- Q.4. (a) State and Explain the Various possible faults in transformer. Why the faults are less in transformer than the generators? [7]
- (b) Describe with the help of a neat diagram the connections of differential protection of transformer. A 3-phase 33/6.6 KV star/delta connected transformer is protected by differential system. The CT's on LT side have a ratio of 300/5. Show that the CT's on HT side will have a ratio  $60:5\sqrt{3}$ . [9]

#### OR

- Q.4. (a) Explain the Buchholz relay with reference to
- Principle of operation
  - Installations. [7]
  - Difficulties.
  - Merits.
  - Limitations.

- (b) Draw neat circuit diagram showing high impedance three-phase bus bar differential protection and what are the difficulties encountered in their protection?

### UNIT – V

- Q.5. (a) Explain how an impedance relay is used for distance protection, obtain its operating characteristics. Draw its operating characteristics on R-X diagram. [8]
- (b) Explain with diagram the working principle of MHO relay. Deduce the torque equation of the same. [8]

### OR

- Q.5. (a) Describe the scheme for single phasing protection of Induction Motor. [6]
- (b) Explain abnormal conditions and possible failure of induction Motors. [5]
- (c) What is phase reversal? What is its effect? How it is prevented in induction Motors. [5]
-