

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech. (Electronics Engg.) (2012 Onwards)
B.Tech. (ECE)/(Electronics & Computer Engg.)
(ETE) (2011 Onwards) (Sem.-3)
NETWORK ANALYSIS AND SYNTHESIS
Subject Code : BTEC-303
Paper ID : [A1127]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

SECTION-A

1. Write briefly :

- (a) Explain the term Network Synthesis.
- (b) What are Dependent Sources ? Explain with example.
- (c) Define Superposition theorem.
- (d) State and explain Maximum Power Theorem.
- (e) Define Ideal Filter.
- (f) Differentiate between loop and mesh.
- (g) What is the need of Laplace transform ?
- (h) List the demerits of m-derived filters.
- (i) Define positive real function.
- (j) How will you define transfer function? Explain.

SECTION-B

2. State and prove convolution theorem.
3. An impedance function is given by

$$Z(s) = \frac{2(s + 1)(s + 3)}{(s + 2)(s + 4)}$$

Find the RL representation of foster first form of network.

4. (a) How can you remove a pole at infinity ?
(b) How can you remove a pole at zero ?
(c) What are the necessary conditions of stability of a network function ?
5. Discuss realizability conditions for impedance synthesis of RL and RC circuits.
6. How is open circuit (Z) parameters converted into short circuit (Y) - parameters? Show all steps involved and discuss conditions for reciprocity and symmetry.

SECTION-C

7. Define driving point impedance and admittance. State restrictions on location of poles and zeros in driving point functions. What are the various necessary conditions for transfer condition ?
8. Design a low pass prototype T-section filter having cut off frequency of 2 KHz to operate with a terminated load resistance of 500 ohm.
9. Draw m-derived high pass filter. Plot characteristic impedance, phase shift and attenuation *verses* frequency for m-derived filter.

://questionpaperresult.c