

5E5102

Roll No. _____

Total No of Pages: **2**

5E5102

B. Tech. V Sem. (Main/Back) Exam., Nov.-Dec.-2016
Computer Engineering
5CS2A Digital Logic Design

Time: 3 Hours

Maximum Marks: 80
Min. Passing Marks Main: 26
Min. Passing Marks Back: 24

Instructions to Candidates:

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.

Units of quantities used/calculated must be stated clearly.

*Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)*

1. NIL _____

2. NIL _____

UNIT - I

Q.1 Explain Hardware Description Languages and their use in digital logic design in detail along with their application areas. [16]

OR

Q.1 (a) Describe scalar data types & operations in VHDL. [8]

(b) Explain scalar data types & operations in VHDL. [8]

UNIT - II

Q.2 Write Technical notes on following -

(a) Packages & Use Clauses in VHDL. [8]

(b) Components & configurations in VHDL. [8]

OR

- Q.2 What are concurrent statements in VHDL. Also explain use of VHDL in simulation and synthesis of digital circuits with example. [16]

UNIT – III

- Q.3 (a) Write and explain design steps for synchronous sequential circuits. [8]
(b) Write short note on programmable logic devices in detail. [8]

OR

- Q.3 Explain the process of converting ASM charts to hardware and also explain Algorithmic state charts in detail along with concept of set-up time and hold time. [16]

UNIT – IV

- Q.4 Explain in detail dynamic hazards, function hazards, and essential hazards in combinational networks. rtuonline.com [16]

OR

- Q.4 (a) What are stable and unstable states. Explain the concept of races and race-free assignments in detail. [10]
(b) Write short note on compatibility and state reduction procedure. [6]

UNIT – V

- Q.5 Explain following incorporate with field programmable gate arrays. [8×2=16]
(a) Logic elements & programmability.
(b) Interconnect structures & programmability.

OR

- Q.5 Write short notes on - [8×2=16]
(a) Extended Logic elements in FPGA.
(b) Flash Memory & anti-fuse configuration in FPGA.