

3E1614

Roll No. _____

[Total No. of Pages : 3]

3E1614

B.Tech. III Semester (Main/Back) Examination, Dec. - 2016
Applied Elect. & Inst. Engg.
3AI3 Circuit Analysis & Synthesis
EC, EI, EX, AI, BM

Time : 3 Hours

Maximum Marks : 80


Min. Passing Marks : 26

Instructions to Candidates:

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Unit - I

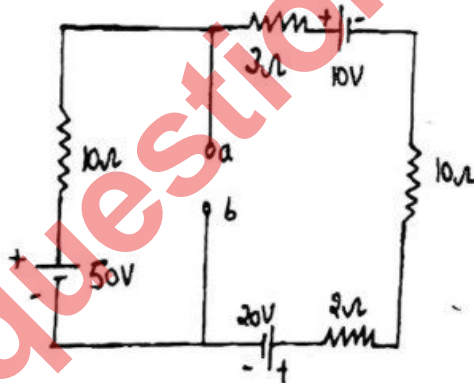
1. a) State and explain Thevenin's theorem with the help of suitable example. (8)
b) Using superposition theorem, find the current through a link is to be connected between terminals a-b. Assume the link resistance to be zero.



(8)

OR

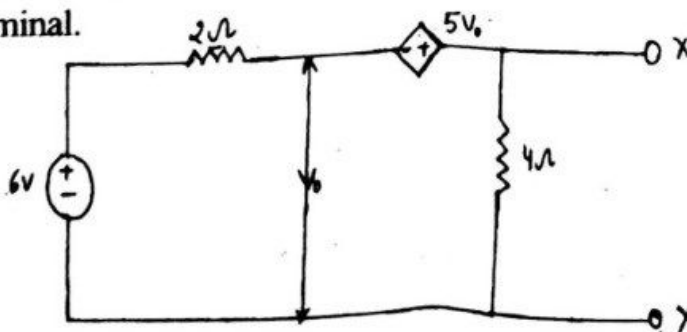1. a) State and prove maximum power transfer theorem. (8)
b) Find the Norton's equivalent of the circuit shown in figure at the left of X-Y terminal. (8)




(1)

[Contd....

Unit - II

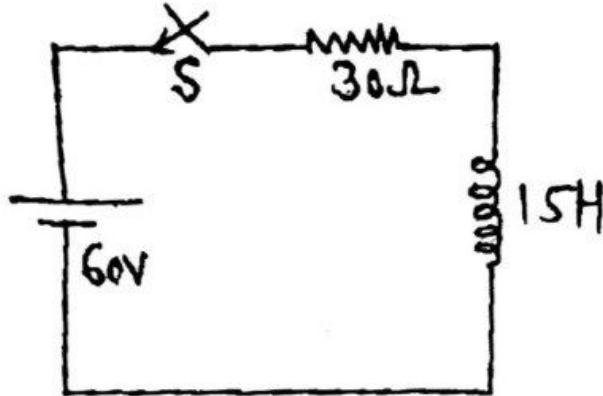2. a) A series RL circuit with $R = 30\Omega$ and $L = 15\text{ H}$ has a constant voltage $V = 60\text{ V}$ applied at $t = 0$ as shown in fig. Determine the current i , the voltage across resistor and the voltage across the inductor.



(8)

- b) Explain different types of functions used in transient analysis.

(8)

OR

2. a) Find the transient responses of :

a) Series R-L

b) Series R-C circuit having sinusoidal excitation

(8)


- b) The step voltage applied to a series R-L circuit is 36 V with $R = 15\Omega$. Determine the value of inductance L required to make the current of 1.0 A at $250\ \mu\text{ sec}$. Assume the initial current is zero.

(8)

Unit - III

3. a) Find $Z(s)$ for the following network.

(8)

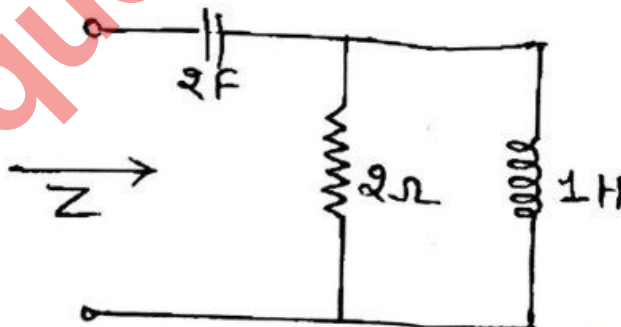

- b) Explain the relationship between pole position and stability.

(8)

OR

3. a) Obtain the pole zero diagram of the given function and obtain the time domain response.


$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)}$$

(8)

- b) Check whether the following polynomial $P(S) = S^4 + S^3 + 2S^2 + 2S + 3$ is stable or not comment on your findings. (8)

Unit - IV

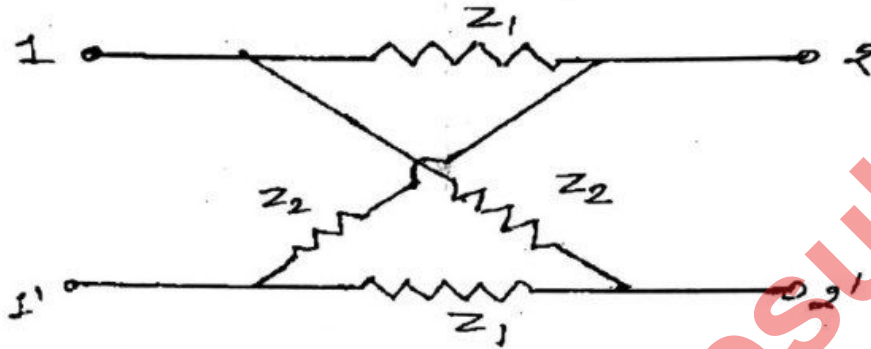
4. a) For the lattice two port network of fig. Find the image impedance and the image transfer constant. (8)



- b) Derive Z-parameters in terms of hybrid parameters. (8)

OR

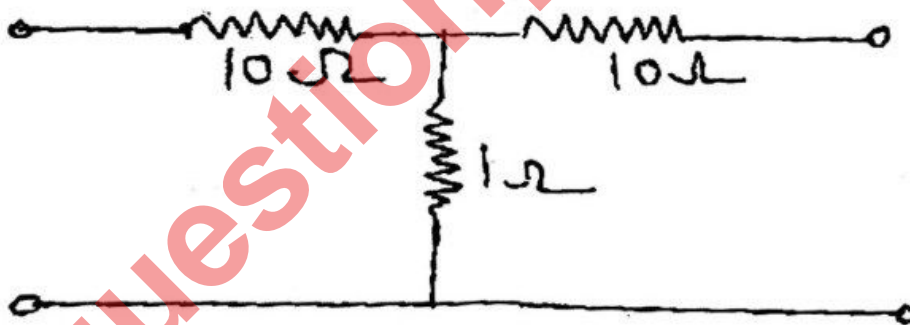4. a) Derive the condition for reciprocity and symmetry in case of ABCD parameters. (8)
- b) Two identical T section, as one shown in fig. are connected in cascade. Determine the Z-parameters of the combination. (8)



Unit - V

5. An impedance is given by $Z(s) = \frac{8(S^2 + 1)(S^2 + 3)}{5(S^2 + 2)(S^2 + 4)}$ Realise the network in Foster - I, II and cauer - I, II form. (16)

OR

5. Realise the function $z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$ in both the cauer and foster forms of LC networks. (16)

