

**7E4048**

Roll No. \_\_\_\_\_

[Total No. of Pages : 3]

**7E4048**

**B.Tech.VII Semester (Main/Back) Examination - 2013**  
**Electronics & Comm.**  
**7EC5 VLSI Design**

Time : 3 Hours

Maximum Marks : 80

Min. Passing Marks : 24

**Instructions to Candidates:**

Attempt any **five** questions, selecting **one** question from each **unit**. All questions carry **equal** marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.)

**Unit - I**

1. a) What are the types of MOSFETs. Draw the schematic diagrams and circuit symbols for all. (4)
- b) Explain the operation of enhancement NMOS using suitable diagrams. (9)  
Also draw the characteristics and justify that it is a voltage controlled current device after seeing the characteristics. (3)

**OR**

1. a) Explain the NMOS fabrication process with the help of neat diagrams (8)
- b) Write the steps to fabricate n-well CMOS (NOT the diagrams) (3)
- c) Write a short note on "depletion mode MOSFET". (5)

**Unit - II**

2. a) Derive  $I_{ds}-V_{ds}$  relationship for MOSFET. (8)

Also prove that the drain current  $I_D = C(1 + \lambda V_{DS})$  in case of channel length

modulation. Where  $C = \frac{1}{2} K_n' \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$ ,  $\lambda$  = process technology parameter

(4)

- b) The NMOS device with  $V_t = 0.7V$  has its source terminal grounded and a 1.3v is applied to gate. The device has  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $W = 10 \mu m$ ,  $L = 1 \mu m$ . Find the value of drain current for  $V_D = 3V$ . (4)

OR


2. a) Prove that the pull-up to pull-down ratio for a NMOS inverter is 4:1 when it is driven by another inverter (8)
- b) Derive the  $\beta_n / \beta_p$  ratio of a CMOS Inverter (8)

Unit - III

3. a) Implement clocked S-R Flip-Flop using CMOS Inverter (8)
- b) Explain transistor sizing of CMOS (5)
- c) Implement OR gate using transmission gate (3)

OR

 3. (a) Realize the following logic expressions using CMOS Inverter
- i)  $AB + \bar{A}\bar{B}$
- ii)  $AB\bar{C} + \bar{A}B.C$
- iii)  $AB\bar{C}D$
- iv)  $AB + BC + AC$  (10)
- (b) Find the equivalent (W/L) ratio of NMOS and PMOS transistors in the given CMOS circuit (6)



#### Unit - IV

4. a) Draw the stick diagrams of
- i) 3 i/p NAND gate
  - ii) 3 i/p NOR gate (4+4=8)
- b) Write a short note on "Layout optimization for performance". (8)

#### OR

4. (a) Draw the stick diagram and layout for the following boolean expression  
 $Y = A.B + C.D + E$  (8)
- (b) What is "Euler path"? What is use of it? Explain with a suitable example (8)

#### Unit - V

5. a) What do you meant by VHDL?  
Write a VHDL code for
- i) Full Adder
  - ii) J-K Flip-flop (2+4+4=10)
- b) Distinguish between
- i) Signal and variable
  - ii) Concurrent and sequential Assignment (3+3=6)

#### OR

5. a) Write a VHDL code for
- i) S-R Flip-Flop
  - ii) 4 bits adder using full adder (8)
- b) Explain
- i) Entity declaration (2)
  - ii) Behavioral style of modelling (3)
  - iii) Structural style of modelling (3)