

**7E7084**

Roll No. \_\_\_\_\_

Total No of Pages: **4****7E7084****B. Tech. VII Sem. (Main) Exam., Nov.-Dec.-2016  
Electronics & Communication Engineering  
7EC5A VLSI Design****Time: 3 Hours****Maximum Marks: 80****Min. Passing Marks Main: 26****Min. Passing Marks Back: 24***Instructions to Candidates:*

*Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.*

*Units of quantities used/calculated must be stated clearly.*

*Use of following supporting material is permitted during examination.  
(Mentioned in form No. 205)*

1. NIL2. NIL**UNIT - I**

Q.1 (a) The Process Parameters for an NMOS are

oxide thickness  $t_{ox} = 500\text{\AA}$ substrate doping  $M_A = 10^{16} / \text{cm}^{+3}$ Polysilicon gate doping  $M_D = 10^{20} / \text{cm}^3$ Oxide interface fixed charge density =  $2 \times 10^{10} / \text{cm}^3$ .Calculate the Threshold Voltage  $V_T$  for it.

[10]

(b) Discuss following High order effects in MOSFET -

(i) narrow channel effect

[3]

(ii) sub threshold conduction

[3]

OR

Q.1 (a) Draw all fabrication steps to achieve following inverter (fig. 1)

[8]

 


Fig - 1

Starts the fabrication using n - type substrate. [rtuonline.com](http://rtuonline.com)

(b) Calculate the Junction capacitance at drain end in a NMOS shown in fig - 2 [8]

 


fig - 2

With substrate doping  $N_A = 10^{12} / \text{cm}^3$

drain doping  $N_D = 10^{18} / \text{cm}^3$

Junction depth  $X_j = 0.1 \mu\text{m}$

Drain Pellet is square of size  $w_0 \times w_0 = (0.01 \times 0.01) \mu\text{m}^2$

## UNIT - II

Q.2 (a) Define noise margin for low and noise margin for high. Calculate these value for a CMOS inverter having  $V_{in} = |V_{tp}| = 0.8$ ,  $\frac{K_n}{K_p} = 2.5$ , and supply is  $V_{DD} = 5$  volt. [8]

(b) Draw CMOS logic circuit for realize  $y = \frac{[A(B+C)](DEE)}{ADE(B+C)}$ . Also set the (W/L) of each NMOS and PMOS such that the equivalent ratio of  $\frac{K_n}{K_p} = 4$ . [8]

### OR

Q.2 (a) Draw the edge triggered D - Latch using CMOS logic. [6]

(b) Draw  $4 \times 1$  Mux using transmission gate. Also compare the total no. of transistor required for such Mux using CMOS and TG. [6]

(c) Define power delay product (PDP) and energy delay product (EDP). Discuss why these parameters are called Figure of Merit for logic circuit. [4]

## UNIT - III

Q.3 (a) Draw the Layout using possible Euler path for  $y = (A + BC)(D + E)$  [8]

(b) Draw the  $2 \times 1$  Mux Layout using TG. [8]

### OR

Q.3 (a) What are DRC rules for Layout? State any six DRC rules. Why we need to follow DRC rules when draw layout for any logic circuit? [6]

(b) Draw the Layout for a Half Adder using CMOS logic. [6]

(c) Draw Latch - up formation in CMOS inverter. [4]

### UNIT - IV

Q.4 Draw following & explain their working-

[4×4=16]

- (a) SRAM ccll
- (b) DRAM ccll
- (c)  $y = \overline{(AB+C)}$  using Domino logic
- (d) Any NP (zipper) logic

OR

- Q.4 (a) Explain the pre-charge and evaluation logic and explain zero transfer in detail. [8]  
(b) What is C<sup>2</sup>MOS logic? Draw any logic circuit using it. What are additional advantages of such logic? [8]

### UNIT - V

- Q.5 (a) Write the difference between custom design and FPGA in respect of design time and cost. [8]  
(b) Write VHDL code for 2 input NAND and NOR gate. [8]

OR

Q.5 Write short note on any two -

[2×8=16]

- (i) ASIC Design
  - (ii) VHDL code for FF
  - (iii) Difference between First and Back End design.
-